

CSE231 HW #1

In the book Nilsson, Riedel "*Electric Circuits*" 10th ed. solve the following problems and simulate the ones having (PSPICE|MULTISIM) label using EasyEDA simulation software.

- 3.1
- 3.2
- 3.3
- 3.4
- 3.5
- 3.8
- 3.13
- 3.17
- 3.18
- 3.19
- 3.22
- 3.28
- 3.32
- 3.52
- 3.53
- 3.58
- 3.62
- 3.67
- 3.73
- 3.74

You should solve them on paper, then scan using apps like (Adobe Scan, Cam Scanner, etc.) also add your simulation results to the PDF report.

Deadline 6/11/2020 11:55AM (Noon)

Corresponding Teaching Assistants:

- umit.akkaya@gtu.edu.tr
- m.kilinc@gtu.edu.tr
- sametgul@gtu.edu.tr