

3.1) a) $120 = i_3 \cdot 10$

$i_3 = 12 \text{ A} , i_1 = 4 \text{ A} , i_2 = 8 \text{ A}$

for point a:

$$i_3 - i_2 - i_1 = 12 - 4 - 8$$

$i_3 - i_2 - i_1 = 0$ (The circuit satisfied KCL for point a)

for point b:

$$i_1 + i_2 - i_3 = 4 + 8 - 12 = 0 \quad (\text{The circuit satisfied for point b})$$

b)

for loop 1


$$-120 + (4 \times i_1) + (18 \times i_1) = -120 + (4 + 12) + (18 \times 4) = 0$$

$$\text{for loop 2} \Rightarrow -(18 \times i_1) + (3 \times i_2) + (6 \times i_2) = -(4 + 18) + (8 + 3) + (8 + 6) = 0$$

The circuit satisfied KVL at every loop

a)
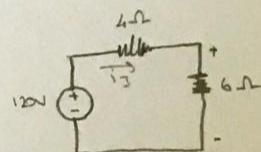
$$\frac{1}{R_{\text{eq}}} = \frac{1}{9} + \frac{1}{18} \Rightarrow R_{\text{eq}} = 6 \Omega$$



KVL for loop 1:

$$-120 + i_3 \cdot (4 + 6) = 0$$

$$i_3 = 12 \text{ A}$$

$$V = 12 + 6 = 18 \text{ V}$$

By applying current dividing

$$i_2 = \frac{i_3 \times 18}{12 + 18} = \frac{8}{27} \text{ A}$$

$$P_{4\Omega} = (i_2)^2 \cdot 4 \Rightarrow 384 \text{ W}$$

$$P_{3\Omega} = (i_2)^2 \cdot 3 = 192 \text{ W}$$

$$P_{6\Omega} = \frac{V^2}{18} = \frac{(18)^2}{18} = 18 \text{ W}$$

$$P_{12\Omega} = (i_3)^2 \cdot 12 = 576 \text{ W}$$

b)

$$P_{\text{deliv}} = 120 \times i_3$$

$$P_{\text{deliv}} = 120 \times 12 \Rightarrow 1440 \text{ W}$$


c)

$$P_{\text{dissipated}} = P_{4\Omega} + P_{12\Omega} + P_{3\Omega} + P_{6\Omega}$$


$$= 576 + 18 + 192 + 384$$

$$= 1440 \text{ W}$$

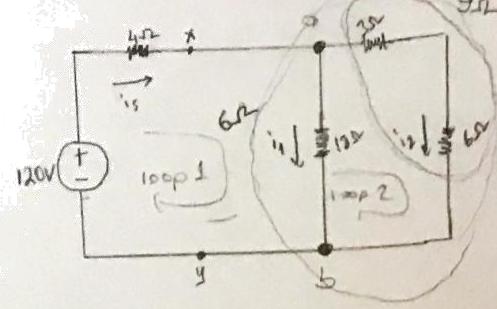
$$\Rightarrow P_{\text{delivered}} = P_{\text{dissipated}}$$




3.3

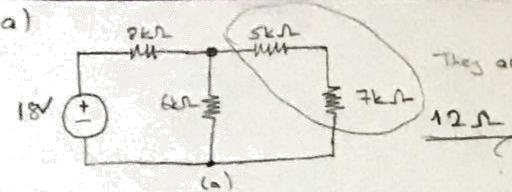

They are in a series.

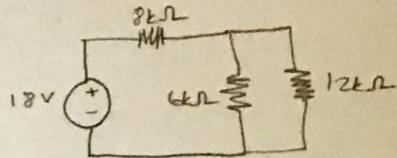

b)

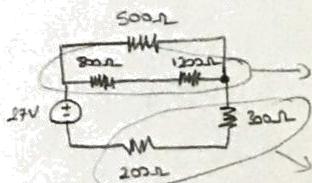


$$R_{eq} = 800 + 1200 = 2000 \Omega$$


They are in a series.

$$R_{eq} = 300 + 200 = 500 \Omega$$

They are in a series.

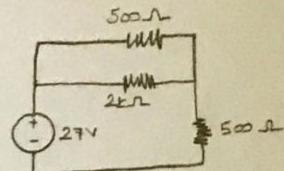


c)

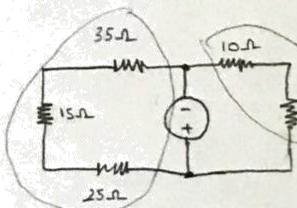

They are in a series.


$$R_{eq} = 10 + 40 = 50 \Omega$$

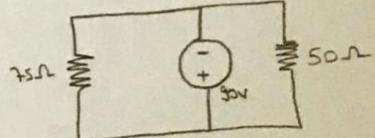

They are in a series.


$$R_{eq} = 35 + 15 + 25 = 75 \Omega$$

d)

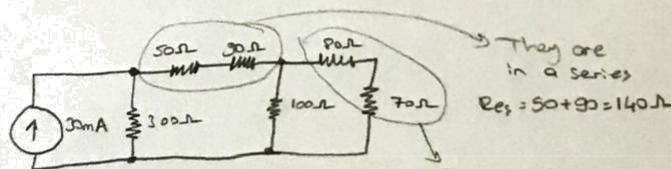

They are in a series.


$$R_{eq} = 50 + 90 = 140 \Omega$$

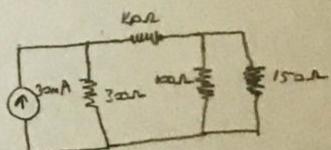

They are in a series.


$$R_{eq} = 80 + 70 = 150 \Omega$$

3.4

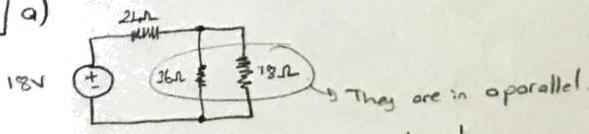


They are in a parallel.
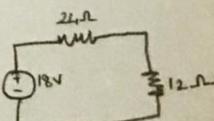
$$\frac{1}{R_{eq}} = \frac{1}{36} + \frac{1}{18}$$




b)

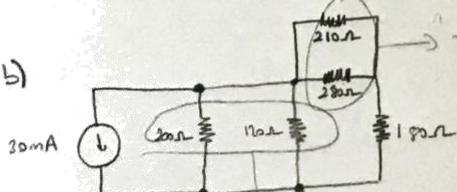

They are in a parallel.


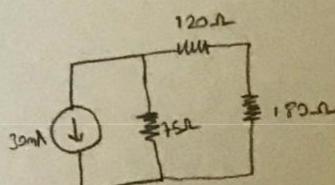
$$\frac{1}{R_{eq}} = \frac{1}{210} + \frac{1}{280} \Rightarrow 120 \Omega = R_{eq}$$





They are in a parallel.

$$\frac{1}{R_{eq}} = \frac{1}{200} + \frac{1}{120} \Rightarrow R_{eq} = 75 \Omega$$

c)

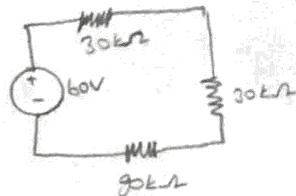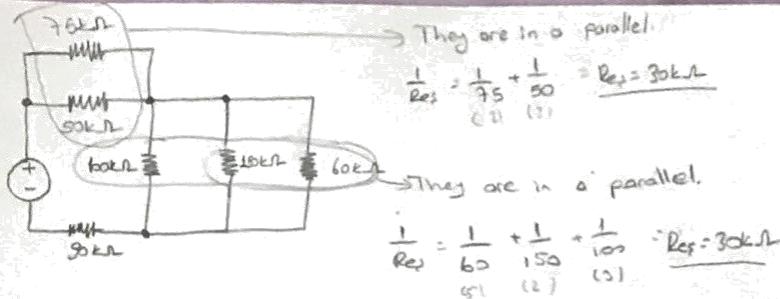

d)

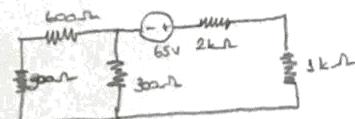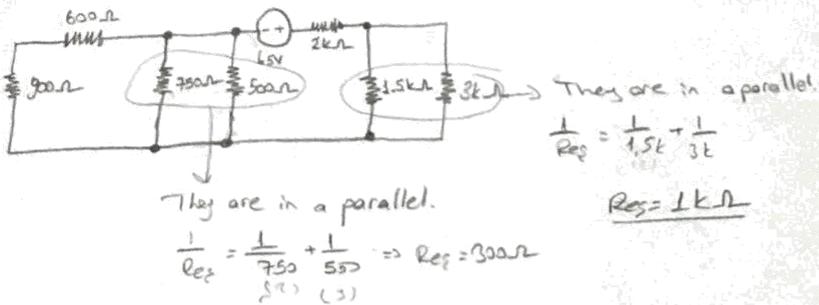

3-5

a)


$$R_{eq} = 5k\Omega + 7k\Omega = 12k\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{12k} + \frac{1}{6k} = R_{eq} = 4k\Omega$$

$$R_{eq} = 8+4 = 12k\Omega$$

$$i = \frac{18V}{12k\Omega} = 1.5mA$$

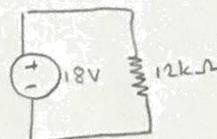
$$P = i \cdot v = 1.5mA \times 18V = 27mW$$



$$b) R = 800\Omega + 1200\Omega = 2000\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{2000} + \frac{1}{500} = R_{eq} = 400\Omega$$
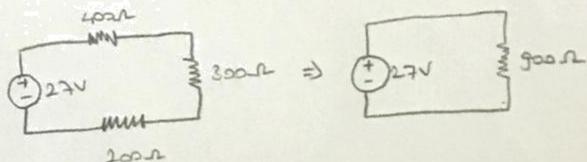
$$R_{eq} = 400 + 300 + 200\Omega \Rightarrow R_{eq} = 900\Omega$$




$$i = \frac{27V}{900\Omega} = 30mA$$

$$P = i \cdot v = 30mA \times 27V = 810mW$$

$$c) R_{eq} = 35\Omega + 15\Omega + 25\Omega = 75\Omega$$

$$R_{eq} = 10\Omega + 40\Omega = 50\Omega$$
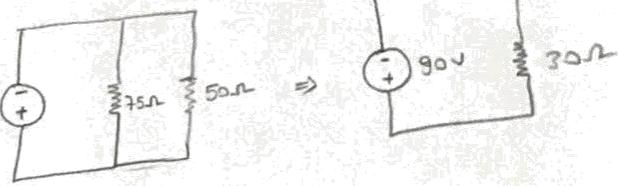
$$\frac{1}{R_{eq}} = \frac{1}{50} + \frac{1}{75} \Rightarrow 30\Omega = R_{eq}$$



$$i = \frac{90V}{30\Omega} = 3A$$

$$P = 3A \cdot 90V = 270 \text{ mW}$$

d)

$$R_{eq} = 50 + 30 = 140\Omega$$

$$R_{eq} = 80 + 70 = 150\Omega$$


$$\frac{1}{R_{eq}} = \frac{1}{100} + \frac{1}{150} \Rightarrow R_{eq} = 60\Omega$$

$$R_{eq} = 140 + 60\Omega = 200\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{200} + \frac{1}{300} = 120\Omega = R_{eq}$$

$$V = i \cdot R \Rightarrow 30\text{mA} \cdot 120 = V = 3.6V$$
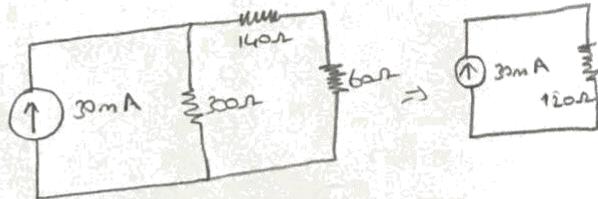
$$P = i \cdot V = 30\text{mA} \cdot (3.6V) \Rightarrow 108 \text{ mW}$$



3.8

$$a) R_{ab} = 24 + (90||60) + 12 = 24 + 36 + 12 = 72\Omega$$

$$\frac{1}{R_{ab}} = \frac{1}{90} + \frac{1}{60} \Rightarrow R_{ab} = 36\Omega$$

$$b) R_{ab} = [(4k + 6k + 2k)||18k] + 5.2k = 4.8k + 5.2k = 10k\Omega$$

$$12k||18k \quad \frac{1}{R_{ab}} = \frac{1}{12} + \frac{1}{18} \Rightarrow R_{ab} = 4.8k$$

$$c) R_{ab} = 1200||720||(320+480) = 288\Omega$$


$$\left(\frac{1}{R_{ab}} = \frac{1}{1200} + \frac{1}{720} + \frac{1}{800} \right) \quad R_{ab} = \frac{720 \cdot 800}{25} = 288\Omega$$

3.13

$$I = \frac{20R_2}{R_2 + 40} \Rightarrow R_2 = 10\Omega$$

$$3 = \frac{20R_e}{40 + R_e} \Rightarrow R_e = \frac{120}{17} \Omega$$

$$17R_c = 120$$

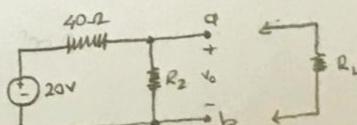


$$\Rightarrow \frac{120}{17} = \frac{10R_L}{10 + R_L} \Rightarrow 170R_L = 1200 + 120R_L$$

$$50R_L = 1200$$

$$R_L = 24\Omega$$

3.17 a)

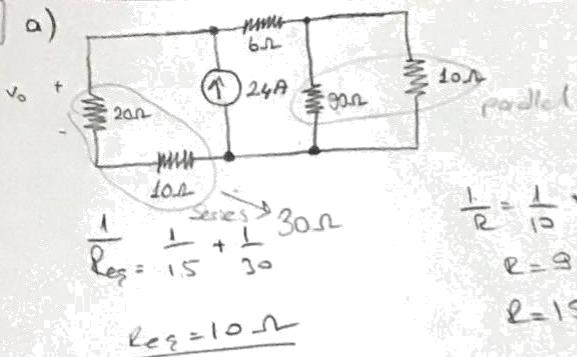

$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{20}$$

$$R_{eq} = 10\Omega$$

$$\frac{1}{R} = \frac{1}{10} + \frac{1}{6}$$

$$R = 9\Omega + 6\Omega$$

$$R = 15\Omega$$

$$I_A = 2 \cdot 6 \times 10$$

$$V = 24V$$

$$V_o = V_{20\Omega} = \frac{20}{10+20} (24) = \underline{16V}$$

$$V_{6\Omega} = \frac{9}{6+9} \cdot 24 = \underline{14.4V}$$

$$I_0 = \frac{14.4}{9\Omega} = 0.16A$$

$$b) P_{6\Omega} = \frac{(V_o - V_{6\Omega})^2}{6} = \frac{(24 - 14.4)^2}{6} = \underline{15.36W}$$

$$c) P_{2.4A} = (2.4)(24) = \underline{57.6W}$$

3.18

We can write KCL for main node

$$i_g = i_1 + i_2 + i_3 + i_4$$

$$i_g = 0.6i_2 + i_2 + 2i_2 + 4 \cdot 0.6i_2$$

$$bi_2 = i_g = 50mA$$

$$i_2 = 8.33mA$$

$$i_1 = (0.6)i_2 \Rightarrow 5mA$$

$$i_3 = 2i_2 \Rightarrow 16.67mA$$

$$i_4 = 4i_1 = 20mA$$

$$R_1 = \frac{25V}{i_1} \Rightarrow R_1 = 5k\Omega$$

$$R_2 = \frac{25V}{i_2} = \frac{25}{0.00833} = 3000 = \underline{3k\Omega = R_L}$$

$$R_3 = \frac{25V}{i_3} = \frac{25}{0.01667} = 1500 = \underline{1.5k\Omega = R_3}$$

$$R_4 = \frac{25V}{i_4} \Rightarrow R_4 = \underline{1.25k\Omega}$$

3.19

$$P = \frac{V}{I} \Rightarrow I = \frac{P}{V} \Rightarrow \frac{80W}{24V} = 3.33A$$

$$R_2 = \frac{V_2}{I} \Rightarrow \frac{5V}{3.33A} = 1.5\Omega$$

$$R_1 = \frac{V_1 - V_2}{I} \Rightarrow \frac{12V - 5V}{3.33A} = 2.1\Omega$$

$$R_3 = \frac{V_3}{I} = \frac{12V}{3.33A} = 3.6\Omega$$

We use

Ohm's Law

to calculate the resistors

3.22

a)

$$i_g = V_0 G_1 + V_0 G_2 + V_0 G_3 + \dots + V_0 G_n$$

$$i_g = V_0 (G_1 + G_2 + \dots + G_n)$$

$$V_0 = \frac{i_g}{G_1 + G_2 + \dots + G_n} \quad (i_k = V_0 G_k)$$

$$\text{or } \frac{i_k}{G_k} = \frac{i_g}{G_1 + G_2 + G_3 + \dots + G_n} \Rightarrow i_k = \frac{i_g G_k}{G_1 + G_2 + \dots + G_n}$$

b)

$$i_s = \frac{40 \cdot \frac{1}{5}}{\frac{1}{0.5} + \frac{1}{5} + \frac{1}{8} + \frac{1}{10} + \frac{1}{20} + \frac{1}{40}} \Rightarrow i_s = \frac{8}{\frac{5}{2}}$$

$$i_s = \frac{16}{5} = 3.2A$$

3.28

$$a) V_{6k} = \frac{6}{6+2} \cdot \frac{(18)^3}{84} = \frac{27}{2} = 13.5V$$

$$V_{3k} = \frac{3}{3+9} \cdot \frac{18^3}{124} = \frac{9}{2} = 4.5V$$


$$\left. \begin{aligned} V_x &= V_{6k} - V_{3k} \\ &= 13.5 - 4.5 \\ V_x &= 9V \end{aligned} \right\}$$

$$b) V_{6k} = \frac{6^3}{84} \cdot (V_s) \Rightarrow V_{6k} = 0.75(V_s)$$

$$V_{3k} = \frac{3}{12} (V_s) \Rightarrow V_{3k} = 0.25(V_s)$$

$$\left. \begin{aligned} V_x &= V_{6k} - V_{3k} \\ &= 0.75(V_s) - 0.25(V_s) \\ V_x &= 0.5(V_s) \end{aligned} \right\}$$

3.32

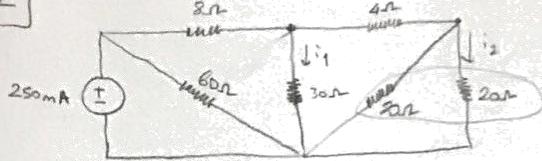

parallel

$$\frac{1}{R} = \frac{1}{20} + \frac{1}{80} \Rightarrow R = 16\Omega$$

$$R = 16 + 4 = 20\Omega$$

We find current division in 8Ω resistor

$$i_{8\Omega} = \frac{15\Omega}{20} \cdot (0.25)$$

$$\frac{1}{R} = \frac{1}{20} + \frac{1}{30} \Rightarrow R = 12\Omega$$

$$R = 12\Omega + 8\Omega = 20\Omega$$

$$V_R = 0.1875 = 187.5\text{ mA}$$

$$\frac{1}{R} = \frac{1}{60} + \frac{1}{20} \Rightarrow R = 15\Omega$$


We use current division to find i_1 from i_8

$$i_1 = \frac{30\Omega}{30} \cdot (i_8) \Rightarrow \frac{12}{36} \cdot (0.1875) = 0.075 = 75\text{ mA}$$

$$i_{4\Omega} = \frac{12}{20} \cdot (0.1875) = 0.1125 = 112.5\text{ mA}$$

$$i_2 = \frac{16}{80\Omega} \cdot (0.1125) = 0.09 = 90\text{ mA}$$

3.52

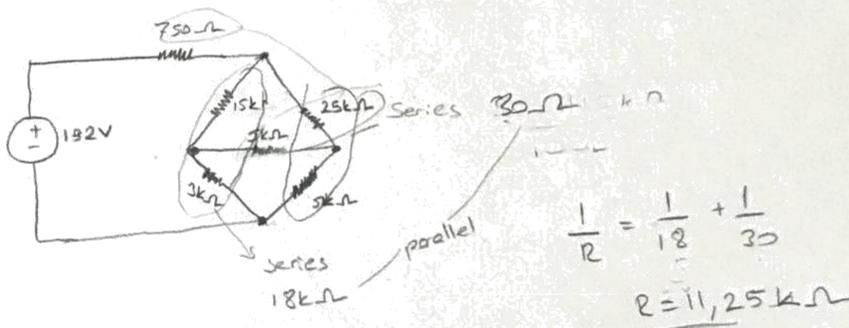

$$\frac{1}{R} = \frac{1}{18} + \frac{1}{30}$$

$$R = 11.25\text{ k}\Omega$$

$$V = iR$$

$$i = \frac{V}{R} \Rightarrow \frac{192}{12000} = 16\text{ mA}$$


$$R = 11.25 + 750\Omega$$

$$R = 12\text{ k}\Omega$$

$$i_{3k} = \frac{11.250}{18000} (0.016) \Rightarrow 10\text{ mA}$$

$$P_{3k} = 3000 \cdot (0.1)^2 = 0.3\text{ W}$$

3.53

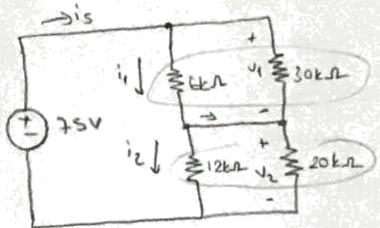

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{30}$$

$$R = 5\text{k}\Omega$$

$$\frac{1}{R} = \frac{1}{12} + \frac{1}{20}$$

$$R = 7.5\text{k}\Omega$$

$$12.5\text{k}\Omega$$

$$i_s = \frac{75}{12.5\text{k}\Omega} = 6\text{mA}$$

$$V_1 = (0.006)(5000) = 30\text{V}$$

$$V_2 = (0.006)(7500) = 45\text{V}$$


$$i_1 = \frac{30}{6000} = 5\text{mA}$$

$$i_2 = \frac{45}{12000} = 3.75\text{mA}$$

$$\left. \begin{array}{l} i_d = i_1 - i_2 \\ i_d = 5 - 3.75 \\ i_d = 1.25\text{mA} \end{array} \right\} i_d = 1.25\text{mA}$$

3.58

a)

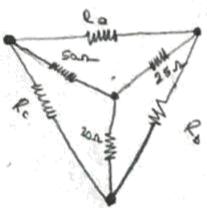

$$R_{ab} = \frac{(25)(30) + (25)(50) + (30)(50)}{30} = \frac{3500}{30} = 116.67\Omega$$

$$R_{bc} = \frac{(25)(30) + (25)(50) + (30)(50)}{50} = \frac{3500}{50} = 70\Omega$$

$$R_{ca} = \frac{(25)(30) + (25)(50) + (30)(50)}{25} = \frac{3500}{25} = 140\Omega$$

$$70 \parallel [50 \parallel 116.67] + [20 \parallel 140] = 30\Omega$$

$$R_{ab} = 13 + 7 + 30 = 50\Omega$$

$$b) R_1 = \frac{(50)(20)}{50+20+30} = 10\Omega$$

$$R_2 = \frac{(50)(30)}{50+20+30} = 15\Omega$$

$$R_{ab} = 50\Omega$$

$$R_3 = \frac{(20)(30)}{50+20+30} = 6\Omega$$

3.62

$$R = 8 + 12 = 20 \Omega$$

$$\Rightarrow \frac{1}{R} = \frac{1}{20} + \frac{1}{60} \Rightarrow R = 15 \Omega$$

$$\Rightarrow 15 + 20 = 35 \Omega$$

$$\Rightarrow \frac{1}{R} = \frac{1}{35} + \frac{1}{140} \Rightarrow R = 28 \Omega$$

$$\Rightarrow 28 + 22 = 50 \Omega$$

$$\frac{1}{R} = \frac{1}{50} + \frac{1}{75} \Rightarrow R = 30 \Omega + 10 = \underline{\underline{40 \Omega}}$$

$$i_g = \frac{240}{40} = \underline{\underline{6 A}}$$


$$i_o = \frac{(6)(50)}{125} = \underline{\underline{2.4 A}}$$

$$i_{140\Omega} = \frac{(6 - 2.4)(35)}{175} = \underline{\underline{0.72 A}}$$


$$P_{140\Omega} = (0.72)^2 \cdot (140) = \underline{\underline{72.576 W}}$$

3.67

a)

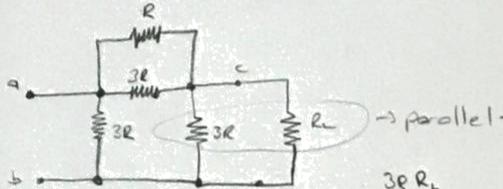
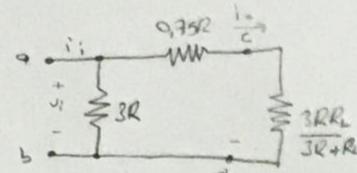
$$\Rightarrow 0.75R + \frac{3RR_L}{3R+R_L} = \frac{2.25R^2 + 3.75RR_L}{3R+R_L}$$



$$\Rightarrow R_{ab} = \frac{3R \left(\frac{2.25R^2 + 3.75RR_L}{3R+R_L} \right)}{3R + \left(\frac{2.25R^2 + 3.75RR_L}{3R+R_L} \right)} = \frac{3R(3R + 5R_L)}{15R + 9R_L}$$

$$\text{If } R = R_L, \text{ we have } R_{ab} = \frac{3R_L \cdot 8R_L}{24R_L} = R_L$$

$$\Rightarrow R_{ab} = R_L$$

$$\text{b) } i_o = \frac{i_i(3R_L)}{4.5R_L} = \frac{1}{1.5} i_i = \frac{1}{1.5} \cdot \frac{v_i}{R_L} \Rightarrow v_o = 0.75R_L i_o = \frac{1}{2} v_i$$

$$\frac{v_o}{v_i} = 0.5$$

3.73 a)

$$V_x = \alpha V_s \quad \alpha = \frac{V_x}{V_s} = \frac{1}{5} = \underline{0.2}$$

$$V_y = \beta V_s \quad \beta = \frac{V_y}{V_s} = \frac{3.75}{5} = \underline{0.75}$$

b)

$$x = (1 - \alpha) p_x = (1 - 0.2)(480) = \underline{384}$$

$$y = (1 - \beta) p_y = (1 - 0.75)(800) = \underline{200}$$

Right corner

3.74


$$x = (1 - \alpha) p_x \Rightarrow \alpha = 1 - \frac{x}{p_x} = 1 - \frac{480}{640} = \underline{0.25}$$

$$V_x = \alpha V_s = (0.25)(8) = \underline{2V}$$


$$y = (1 - \beta) p_y \text{ so } \beta = 1 - \frac{y}{p_y} = 1 - \frac{192}{1024} = \underline{0.8125}$$

$$V_y = \beta V_s = (0.8125)(8) = \underline{6.5V}$$

Şekil 1-P3.1

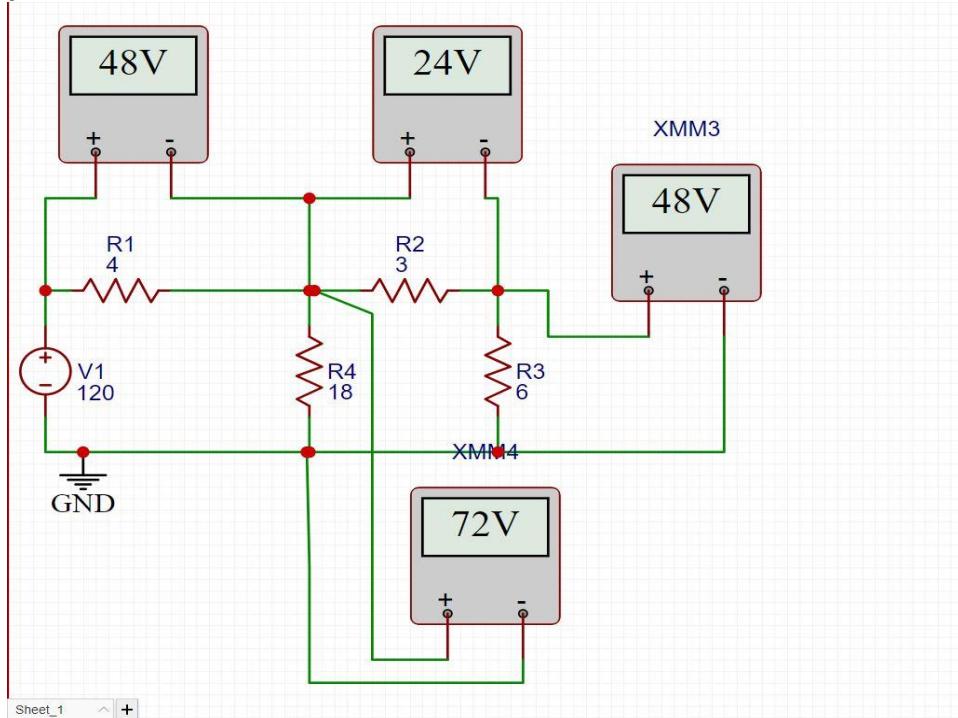


Şekil 2-P3.2

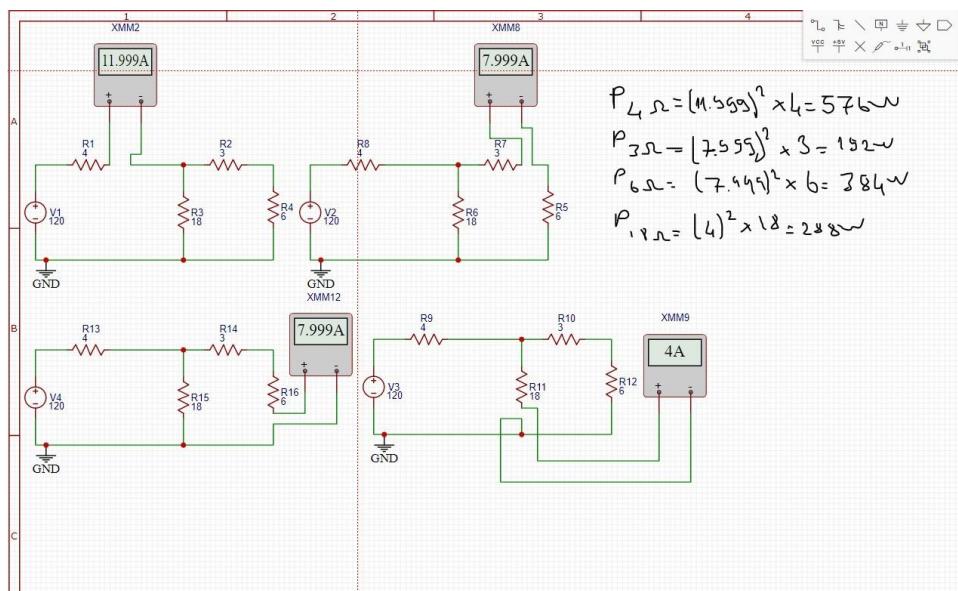

Şekil 3-P3.8A

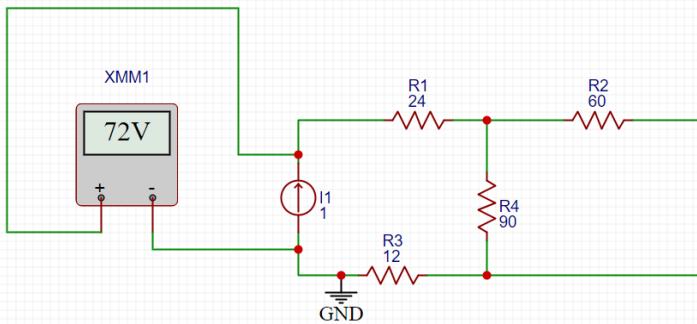
$$R = \frac{V}{I} \Rightarrow \frac{72}{1} = 72 \Omega$$



.tran 10m


Şekil 4-P3.8B
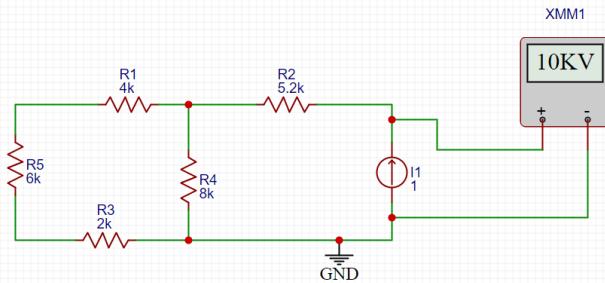
$$R = \frac{V}{I} = \frac{10k}{1} = 10k \Omega$$




.tran 10m

Şekil 5-P3.8C

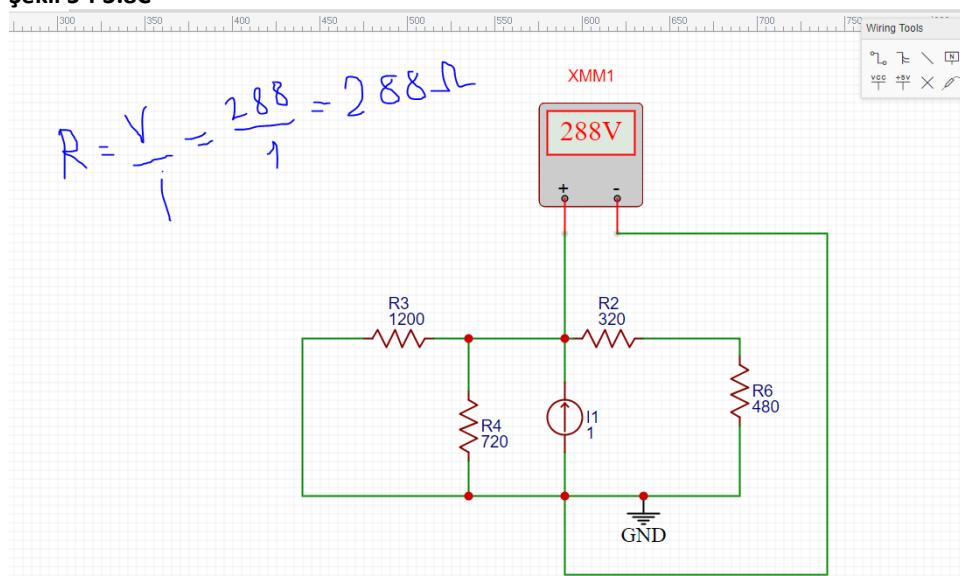


.tran 10m

Şekil 6-P3.13

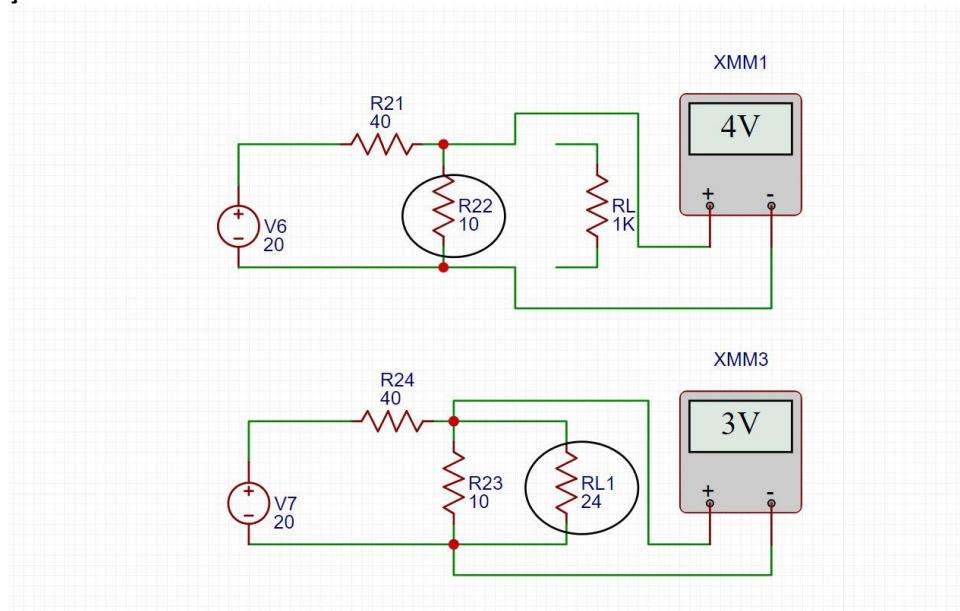


Şekil 7-P3.17A

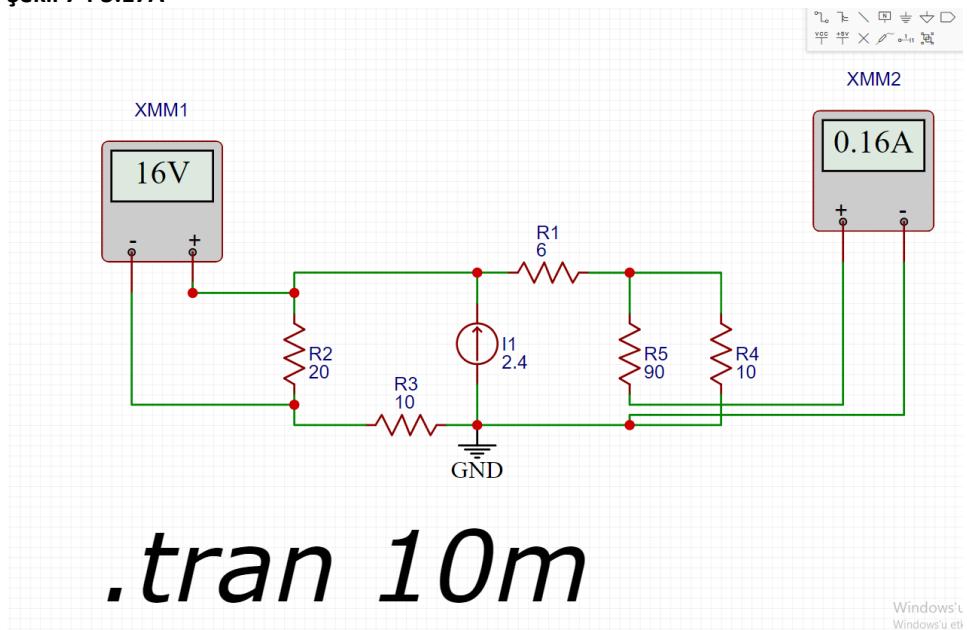

.tran 10m


Windows'ı
Windows'u et

Şekil 8-P3.17B-C

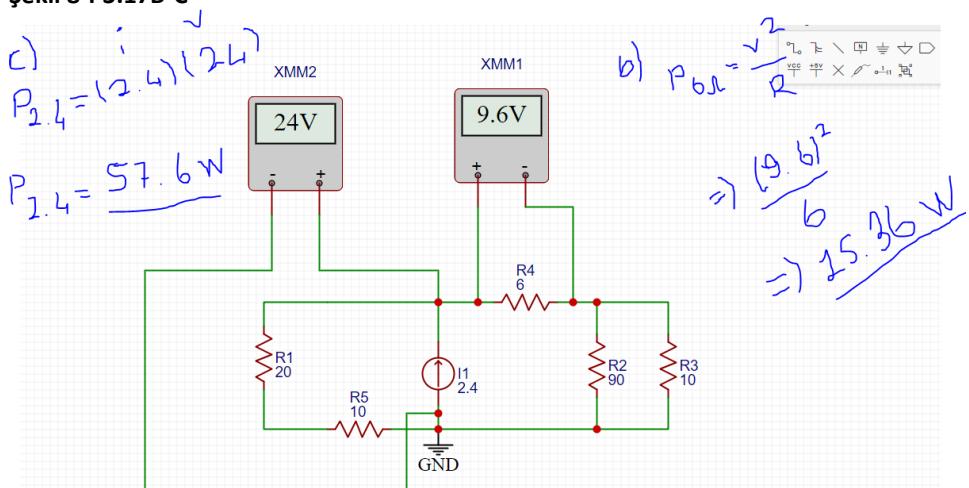


.tran 10m


Şekil 9-P3.18

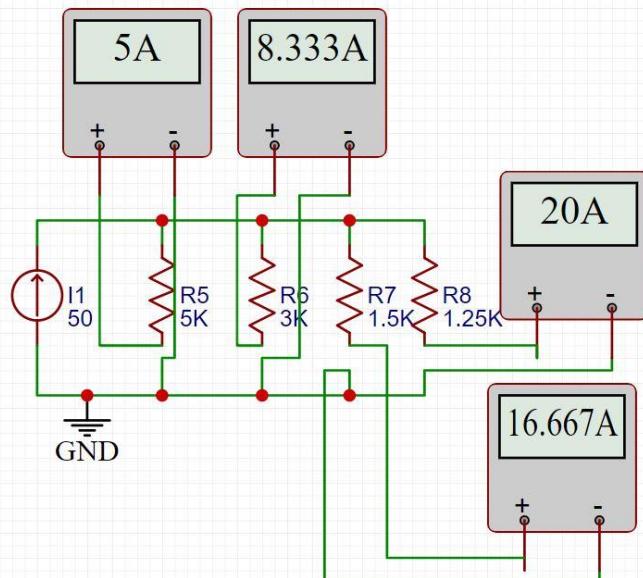

Şekil 10-P3.22

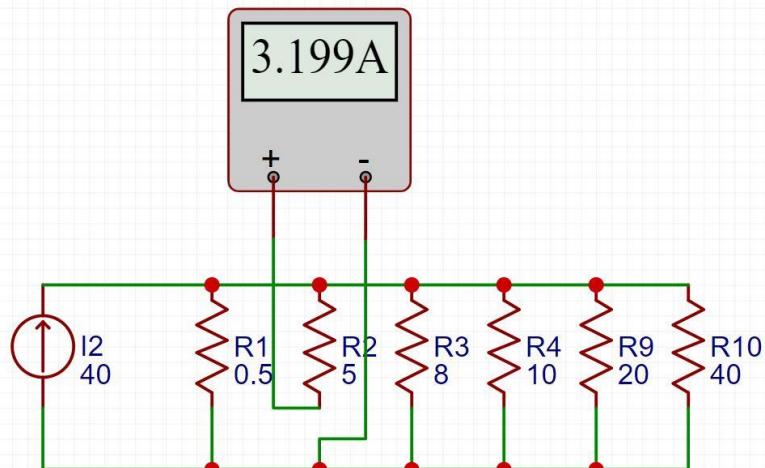


Şekil 11-P3.28

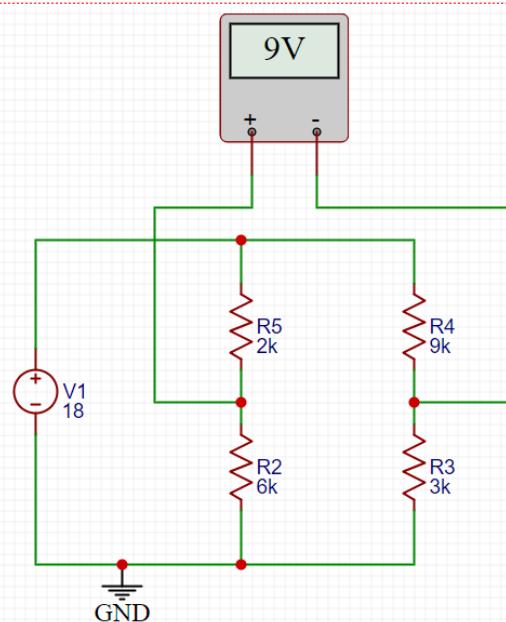


tran 10m

Şekil 12-P3.32

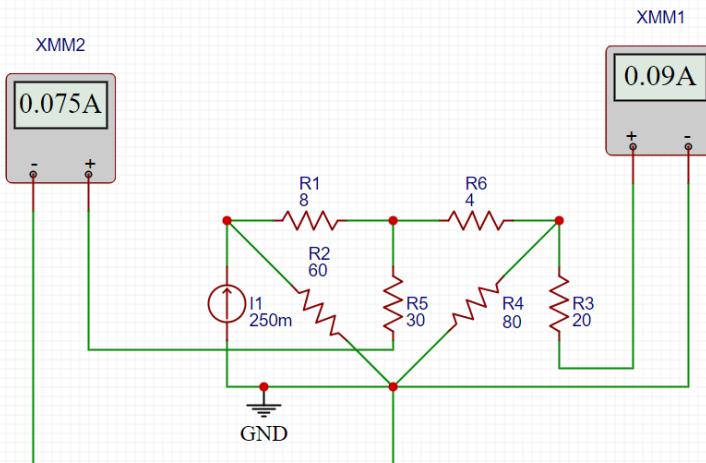

.tran 10m

Şekil 13-P3.52

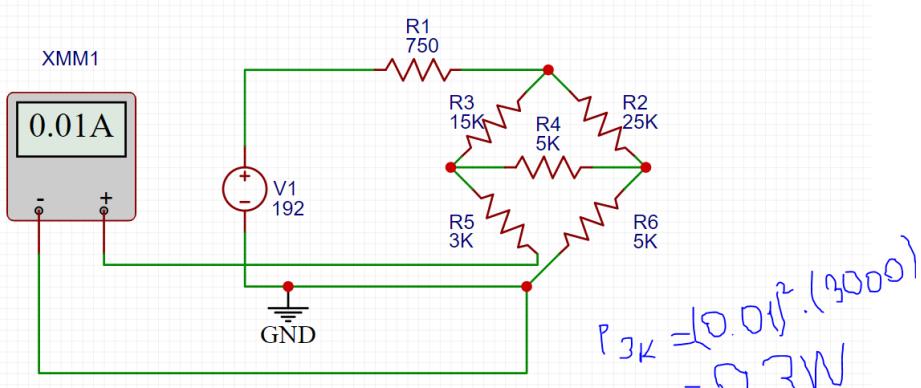

.tran 10m

Şekil 14-P3.62

